

S2

☐ recap☐ how to represent 0/1 in a circuit☐ voltage transfer curves for devices and components☐ MOSFETs and CMOS technology☐ contamination delay, propagation delay.• Recap


- We will learn two types of digital circuits

combinational logic: e.g. ^{adder; rom} given student ID, get score

sequential logic: e.g. a computer.


Both take integer inputs, and yield integer outputs.

The difference is instance vs. sequence.

 

- Both inputs and outputs are represented by binary numbers, representing abstract information (bits).
- The advantage of abstract information representation in the digital abstraction is that it is easy to record and transfer without noise.
- The abstract information is powerful — it can be interpreted as any physical presentation: sounds, images, videos, robotic movement, temperature, floats...
- The 2's complement form of integer representation is commonly used.


How to represent bits in a circuit?

 


Zoom in

- how many integers can the input represent?
- each line is a wire
- a most intuitive way to encode 0/1 - voltage

- Theory

 

- Practice

 

Signal invalid after some resistor in the circuit.


- Solution?

make output range more strict than input range






- Voltage transfer curves

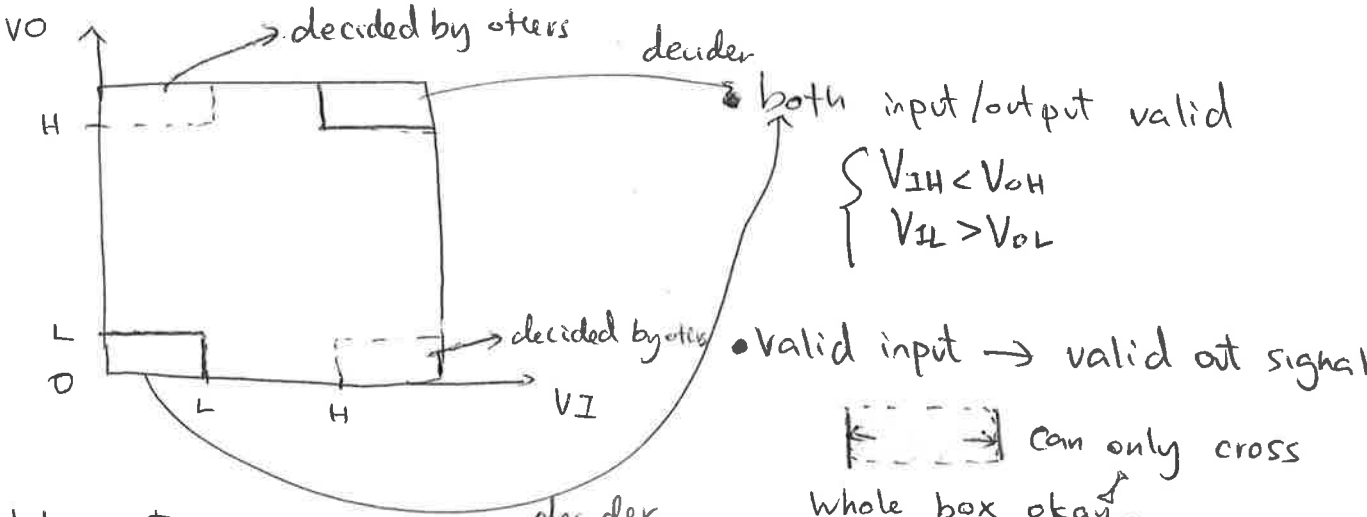


Single bit circuit

 


buffer

inverter

(are there others?)

 

 
buffer's better 'recharge' the input signal (can wires be buffers?)




Inverter.

Contamination delay, propagation delay

Theory

 

Practice (static discipline)

 





MOSFETS and CMOS technology

how does one implement a buffer and a converter?

- Carve silicon (SiO_2)



    
dope with p/n material - S
field effect transistor - FET



PULL-DOWN

PULL-UP

MO

 

PULL-DOWN

PULL-DOWN:

$G > \text{threshold} \rightarrow D \rightarrow 0$


$G \leq \text{threshold} \rightarrow D \text{ disconnected}$

PULL-UP:

$G < \text{threshold} \rightarrow D \rightarrow VDD$

$G \geq \text{threshold} \rightarrow D \text{ disconnected}$

CMOS

 

(B omitted).