

Computation Structures 2014

yuzy

S6 ☐ making state machines

☐ asynchronous circuits & meta stability

State machines


announce quiz. share lecture notes
tsetup
thold

S_0 — start state

- $n(s, i)$ — next state

$o(s, i)$ — output

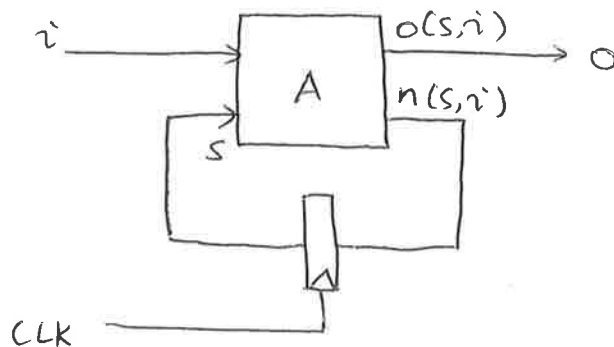- next state will be the state in the next round



- if A implements $o(s, i)$ and $n(s, i)$, then statemachine works
(under the condition that dynamic discipline satisfied)


- e.g. count the number of times a non-zero occurs
for simplicity, just 1-bit count (can extend).
1 if odd, 0 if even.

$X = [0, 1, 0, 2, 3, \dots]$ (for simplicity, 2-bit)

$Y = [0, 1, 1, 0, 1, \dots]$

$$S_0 = 0 \quad n(s, i) = \begin{cases} s & \text{if } i \neq 0 \\ \bar{s} & \text{if } i = 0 \end{cases} \quad o(s, i) = n(s, i)$$

X_1	X_0	S_t	S_{t+1}	O_t
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

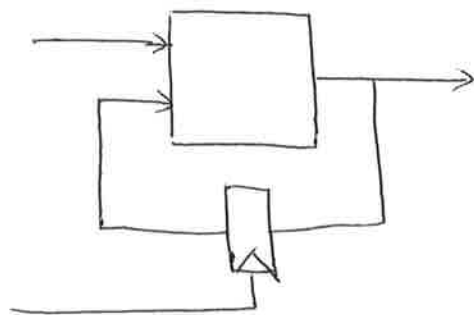


$$S_{t+1} = \bar{X}_1 \bar{X}_0 S_t + \bar{X}_1 X_0 \bar{S}_t + X_1 \bar{X}_0 \bar{S}_t + X_1 X_0 S_t$$

— accumulator → use one adder


Asynchronous circuits & meta-stability

— there are cases when setup and hold time cannot be satisfied.

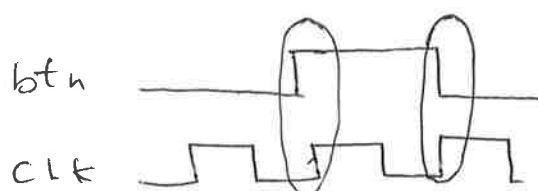
when there are two clocks in a circuit
when there is external signal



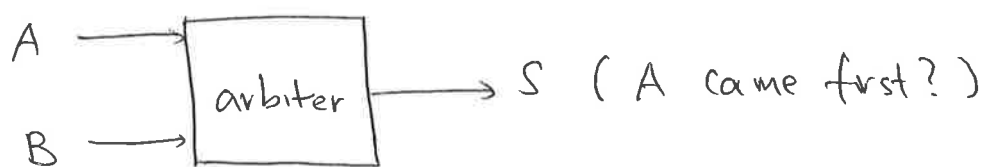
This problem can be reduced to the following problem



it turns out that $\left\{ \begin{array}{l} \text{a correct answer is impossible} \\ \text{an incorrect answer is impossible} \end{array} \right.$


because the output can stay  invalid for infinitely long.

- Analogy

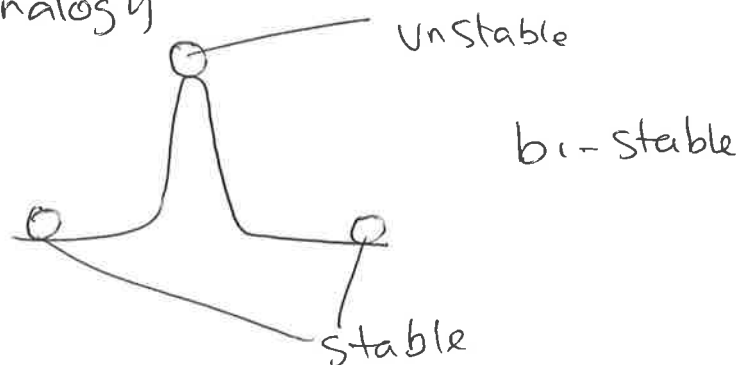


time(unstable) is commonly very small
but there is no guarantee of a bound.

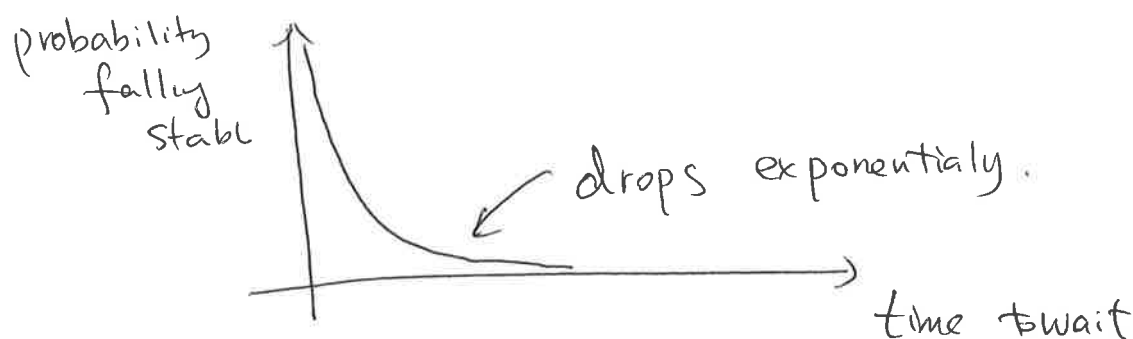
(the sharper, the less likely long staying unstable.)



so the longer to wait, the less likely

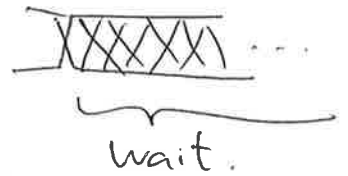

one common solution

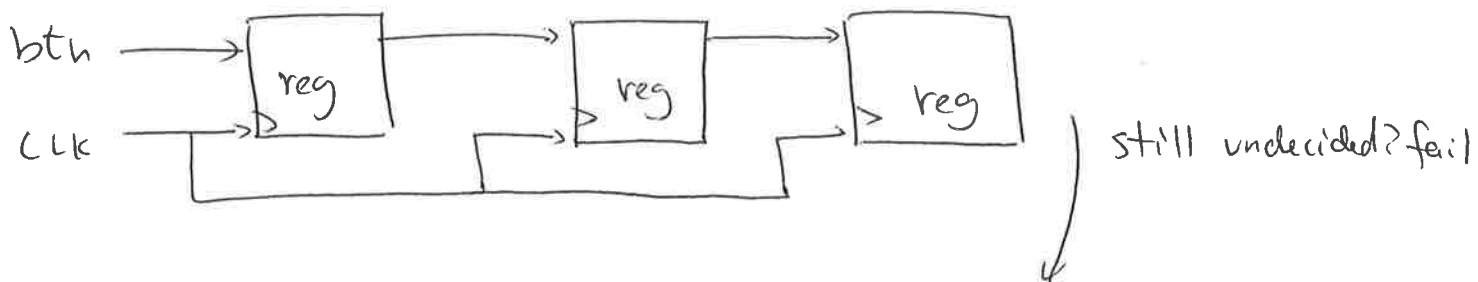

wait 100 ns \longrightarrow 10^{30} years a failure

Take home message = all circuits can fail, but very unlikely